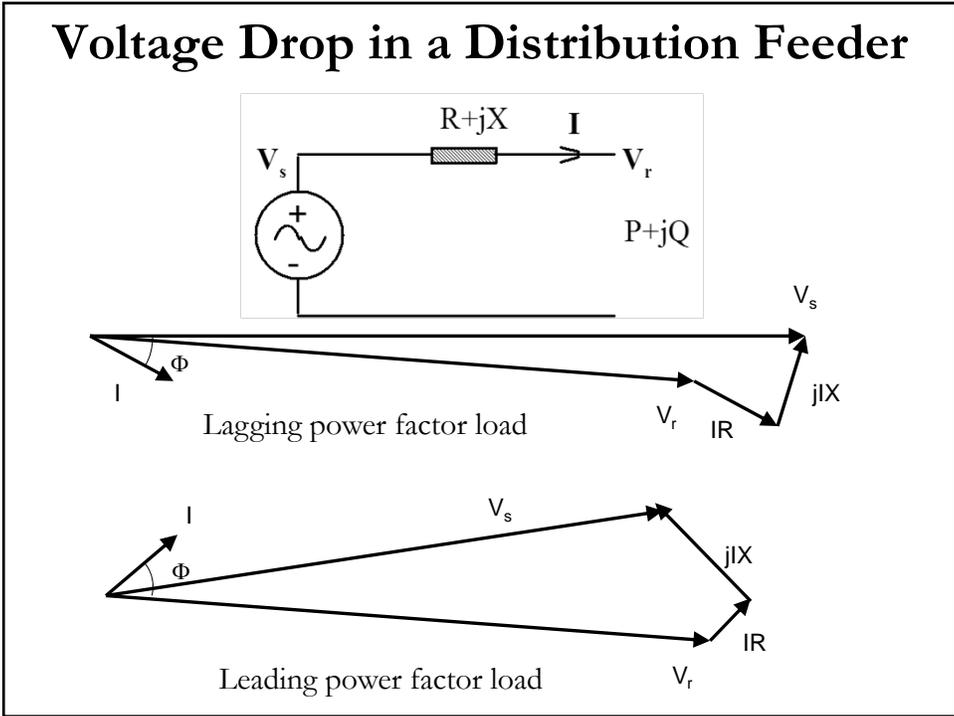


 <p>University of Wollongong</p>	<h1>Voltage Regulation by Distributed Generation</h1>
  <p>endeavour energy power quality & reliability centre</p>	
 <p>Supported by the NSW Government Energy Efficiency Training Program</p>	<p>Kashem Muttaqi</p>

Overview

- ❖ Understanding the concept of voltage regulation by a DG system
- ❖ Method to determine the optimal ratio of real and reactive power injection from DG for maximum voltage support
- ❖ Voltage control approach for DG system to ensure the best performance
- Investigation for network support by considering:
 - The options to maintain acceptable voltage profile,
 - The control strategies to maintain acceptable profiles at lowest cost, and
 - The energy injection for voltage specification.



Voltage Drop Calculations

Normal voltage range: - 6% to +10%

At the receiving end $\mathbf{S} = \mathbf{V}_r \mathbf{I}^* = P + jQ$

Take \mathbf{V}_r to be real so $\mathbf{V}_r^* = \mathbf{V}_r$
 & $\mathbf{I} = \mathbf{S}^* / \mathbf{V}_r^* = (P - jQ) / \mathbf{V}_r$ (1)

Then $\mathbf{V}_s = \mathbf{V}_r + \mathbf{Z}\mathbf{I} = \mathbf{V}_r + (R + jX)(P - jQ) / \mathbf{V}_r$
 $= \left[\mathbf{V}_r + \frac{RP + XQ}{\mathbf{V}_r} \right] + j \left[\frac{XP - RQ}{\mathbf{V}_r} \right]$ (2)

Hence, $\mathbf{V}_s = \mathbf{V}_r + \Delta V_{in} + j\Delta V_{out}$ (3)

Approximation for small voltage drops and Small Resistance

Approximation for small voltage drops

From the diagram, roughly $\Delta V_{in} \rightarrow$ magnitude phase

$\Delta V_{out} \rightarrow$ phase change

$$\text{Hence } V_s - V_r \approx \frac{RP + XQ}{V_r} = RI_{in} + XI_{out} \quad (4)$$

$$\angle V_s - \angle V_r \approx \frac{XP - RQ}{V_r^2} = \frac{XI_{in} - RI_{out}}{V_r} \quad (5)$$

Approximation for small resistance


For higher voltage lines, R is often much smaller than X

$$\text{Hence } V_s - V_r \approx \frac{XQ}{V_r} = XI_{out} \quad (6)$$

$$\angle V_s - \angle V_r \approx \frac{XP}{V_r^2} = \frac{XI_{in}}{V_r} \quad (7)$$

Voltage Regulation: Issue and Concern

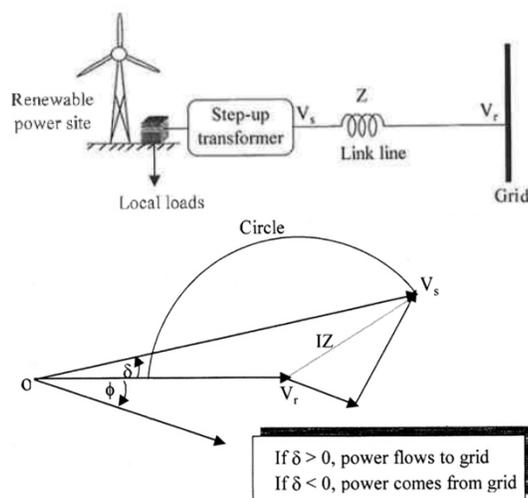
- Voltage regulation is a strong function of the load power factor.
- Voltage regulation is greater for lagging power factor, and the least or even negative for leading power factor.
- If V_r and I are held constant and the power factor of the load is varied from zero lagging to zero leading, the vector V_s will vary such that its end point will lie on a circle since IZ is constant.



Mukund R. Patel, "Wind and Solar Power Systems", CRC Press

Calculation of Voltage Regulation

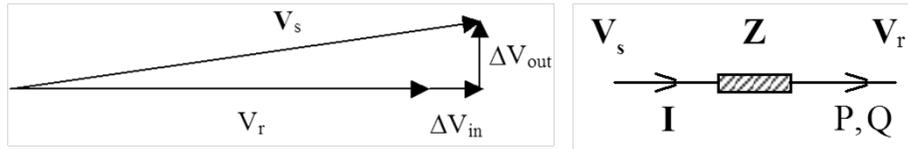- Voltage drop is due to the flow of P, Q in the line and also depend on load demand.




- It has been proved that

$$V_s - V_r \approx \frac{RP + XQ}{V_r} = RI_{in} + XI_{out} = RI\cos\Phi + XI\sin\Phi \quad (1)$$
- Voltage regulation (VR) for a distribution line is

$$\begin{aligned} VR &= (V_{nl} - V_{fl})/V_{fl} = (V_s - V_r)/V_r \\ &= (RI_{in} + XI_{out})/V_r = (RP + XQ)/V_r^2 \end{aligned} \quad (2)$$

Voltage Regulation

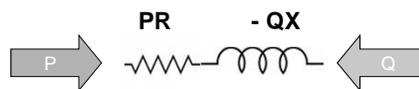- Voltage Regulation (VR) = $(RP + XQ) / V_r^2$
- If P and Q flow in opposite directions...
- QX can cancel out PR!




- No Voltage Drop!

Line Losses

$$\mathbf{V_r I^* = P + jQ} \quad \mathbf{I = (P - jQ) / V_r} \quad \mathbf{I^2 = (P^2 + Q^2) / V_r^2}$$

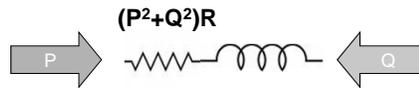- Losses = $I^2 R = R \cdot (P^2 + Q^2) / V_r^2$
- So even if P and Q flow in opposite directions...
- P^2 and Q^2 add together not cancel!



Relation between V, P and Q

- The phase voltage V at a node is a function of real power, P and reactive power, Q at that node, and can be expressed as,

$$\mathbf{V = f(P, Q)} \quad (1)$$

- Therefore, the total differential of V can be written as,

$$\mathbf{dV = \frac{\partial V}{\partial P} \cdot dP + \frac{\partial V}{\partial Q} \cdot dQ} \quad (2)$$

- Equation (2) can be rearranged as,

$$\mathbf{dV = \frac{dP}{(\partial P / \partial V)} + \frac{dQ}{(\partial Q / \partial V)}} \quad (3)$$

- Equation (3) indicates that the change in voltage at a bus depends on the two quantities, which are $\partial P / \partial V$ and $\partial Q / \partial V$.

Relation between V, P and Q (Continued)

- Consider a line with series impedance $R + jX$ and zero shunt admittance.

$$V_s - V_r = \frac{RP + XQ}{V_r} \quad (4) \quad (V_s - V_r)V_r = RP + XQ \quad (5)$$


where V_s is constant, and V_r depends on P and Q.

- From equation (5), we obtain

$$\frac{\partial P}{\partial V_r} = \frac{V_s - 2V_r}{R} \quad (6) \quad \frac{\partial Q}{\partial V_r} = \frac{V_s - 2V_r}{X} \quad (7)$$

- Substituting eqs (6) and (7) into equation (3), we get
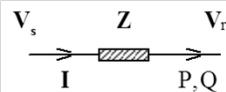
$$dV_r = \frac{dP}{\partial P / \partial V_r} + \frac{dQ}{\partial Q / \partial V_r} = \frac{dP \cdot R + dQ \cdot X}{V_s - 2V_r} \quad (8)$$



Relation between V, P and Q (Continued)

- Voltage change at the receiving-end is

$$dV_r = \frac{dP}{\partial P / \partial V_r} + \frac{dQ}{\partial Q / \partial V_r} = \frac{dP \cdot R + dQ \cdot X}{V_s - 2V_r} \quad (8)$$

- For constant sending-end voltage V_s and for no change in receiving-end voltage ($\Delta V_r = 0$) we have,


$$R dP + X dQ = 0 \Rightarrow R dP = -X dQ \Rightarrow dQ = -\frac{R}{X} dP \quad (9)$$

- This describes the change in Q to maintain the same voltage for a given change in P.
- To have zero voltage drop (zero voltage regulation), inject a sufficient amount of Q so that it satisfy $RP = -XQ$
- The other option, inject P and Q locally so that line power flows will become zero.


$P = P_0(\bar{V})^*$

Voltage correction by DG

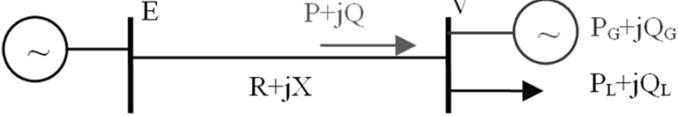- ❖ A power system with DG presence can be expressed by a Thevenin equivalent system



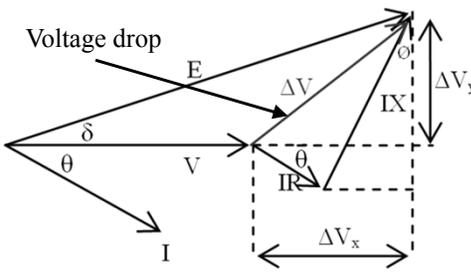- ❖ Phasor diagram of the equivalent system



$$\Delta V_x = \frac{RP + XQ}{V}$$

$$\Delta V_y = \frac{XP - RQ}{V}$$

Voltage correction by DG (cont.)

- ❖ When DG is present

$P = (P_L - P_G)$

$Q = (Q_L - Q_G)$
- ❖ When DG is not present

$P = P_L$

$Q = Q_L$
- ❖ Thus, voltage change by DG (i.e. the change of voltage drop) is


$V^I = V_x^I + jV_y^I$

where:

$V_x^I = \frac{RP_G + XQ_G}{V}$

$V_y^I = \frac{XP_G - RQ_G}{V}$

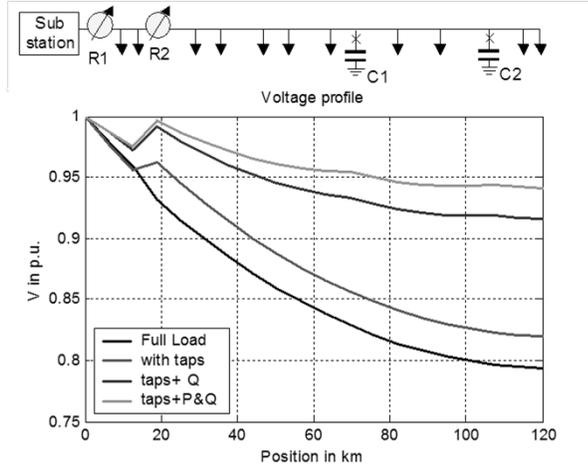Voltage regulators and shunt capacitors for Voltage Correction



• Tap changers can be used to support the downstream voltage but do not respond quickly to load changes.

• Curve 'Full Load' is the profile without regulator or capacitor which is mostly below 0.94 p.u. voltage.

• 'With Taps', the voltage profile moves up with the regulator (R2).

• A set of capacitor banks (C1 and C2), moves the profile to curve 'taps + Q'.

• Introducing generation at the capacitor bank locations is an extreme measure but can also raise the voltage.


Effect of P and Q injections from DG on voltage support

- ❖ Normally, DG is operating with unity power factor (only produces real power).
- ❖ Other (typical) voltage supporting device (i.e. capacitor) produces only reactive power.
- ❖ Yet, it is found that DG operating with both real and reactive power is the best for voltage support.


Combined PQ role for Voltage Support

How to determine optimal injection of P and Q from a DG for maximum voltage support?

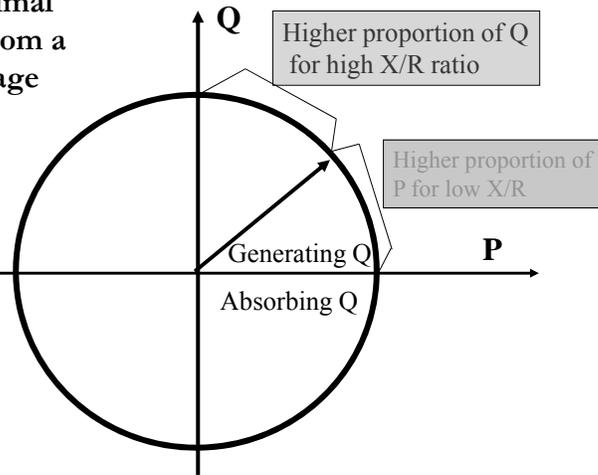- High P effectiveness, high fuel cost: high pf solution
- High Q effect, low fuel cost: low pf solution



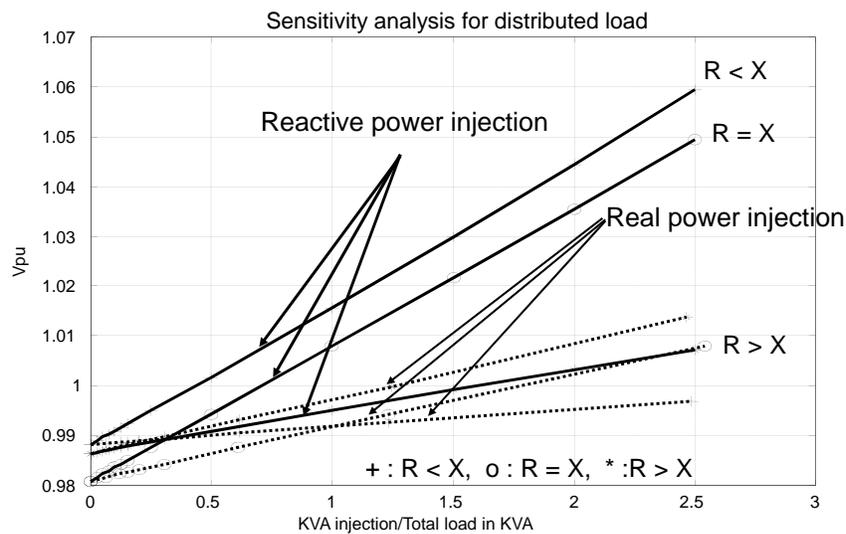What is effective for Acceptable voltage Profile



Determine the optimal operating condition of DG

- ❖ Representing the system by a Thevenin equivalent system looking from DG connection point
- ❖ Developing the relationship between line parameters and bus voltage
- ❖ Examining $\frac{\partial V}{\partial P_{DG}}$ and $\frac{\partial V}{\partial Q_{DG}}$
- ❖ Determining optimal ratio of P_{DG}/Q_{DG}

Voltage sensitivity for a SWER System


$Z_{line} = 1.828 + j0.876$ ohms/km, Source voltage $V_s = 19.1$ kV and source impedance $Z_s = 70.53 + j57.73$ ohms, Load buses $N = 20$, Total load = 352 kW load at 0.8 pf, DG size = 50 kVA

DG mode	P Gen.	Q Gen.	DG Voltage	End Voltage	ΔV at DG connect	ΔV at end point	Sensitivity ratio
No DG	0	0	0.9417	0.9400	-	-	-
DG-P	0.0500	0	0.9750	0.9733	0.0333	0.0333	1.8:1
DG-Q	0	0.0500	0.9602	0.9586	0.0185	0.0186	
DG-PQ	0.0437	0.0240	0.9800	0.9783	0.0383	0.0383	

Note: All are in p.u. and system base is 1MVA

P and Q generations are required at the ratio of 1.8:1 at steady-state situation to improve the network voltage effectively. This performance is a 15% improvement over a pure P solution.

Method of Voltage regulation by DG

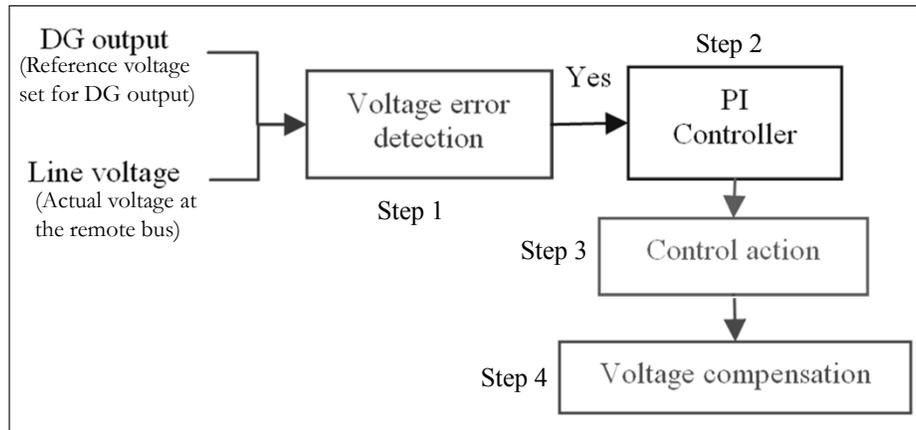

Step 1: Voltage error detection

❖ Voltage error:

$$\Delta V = |V_m| - |V_r| + \varepsilon$$

where: V_m is remote end actual voltage, V_r is reference voltage, and ε is tolerance factor.

❖ V_m is chosen to the voltage at the remote end as the remote bus is the **most voltage-unsafe** bus.

❖ V_m can be obtained by: a) Online measurement

b) Line Drop Compensator

❖ V_r can be set to any desired value (typically it can be set to the lower voltage limit)

Step 2: Derive Control parameters with PI Controller

- ❖ DG controller is adjusted to improve the voltage by injecting both real and reactive power at the optimal ratio of line voltage sensitivity.
- ❖ The output of DG PI Controller can be expressed as:

$$M = K_p \Delta V + K_I \int \Delta V$$

where: M is controller output signal, K_p and K_I are proportional and integral constants, and ΔV is voltage error.


- ❖ K_p and K_I are adjusted to provide sufficient voltage correction.

Step 3 & 4: Control action and Voltage Compensation


- ❖ The voltage compensation is achieved by following control actions:
 - ❖ ‘Switch on’
 - ❖ ‘Increasing output’
 - ❖ ‘Decreasing output’
 - ❖ ‘Switch off’
 - ❖ ‘Doing nothing’

Control Issue with DG

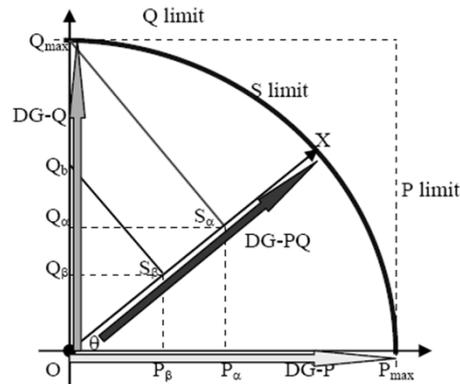- DG controller can be designed for injection of real power, reactive power or real power and reactive power both.
- DG can be operated as DG-P, DG-Q or DG-PQ mode.
- Best-suited control strategy to maintain acceptable profiles at lowest cost should be determined.




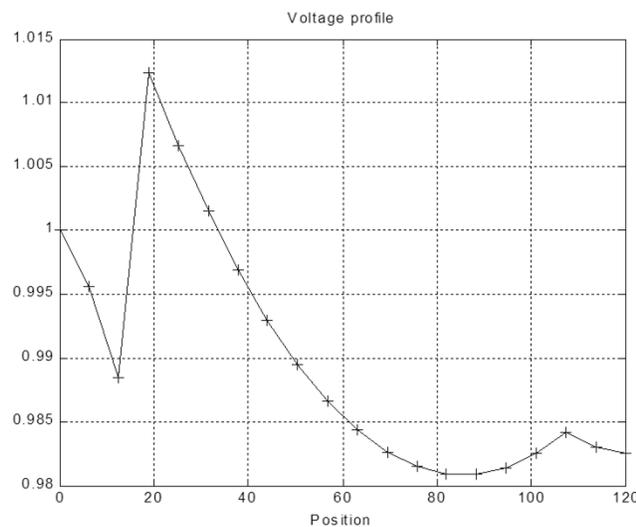Voltage profile with 352 kW load and 100kVA DG-PQ



- Power loss = 8.87 kW and Lowest voltage = 0.9808 p.u.

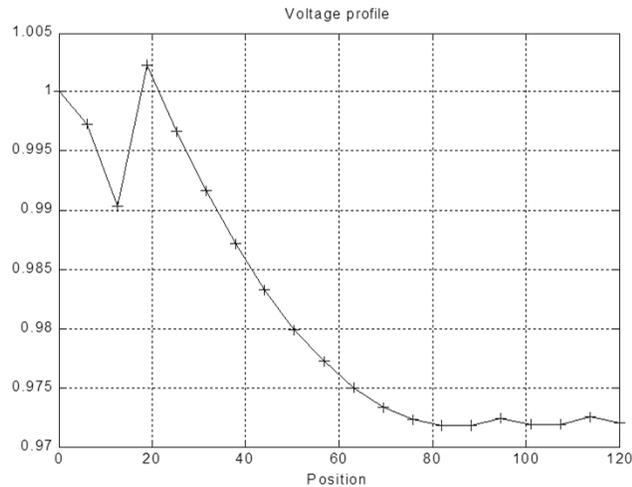
Voltage profile with 352 kW load and 2x50kVA DGs



- Power loss = 8.145 kW and Lowest voltage = 0.9718 p.u.

DG in single DG case provides better voltage support compared to the case of Multiple DGs with same capacity of single DG

Reference level implement priority role

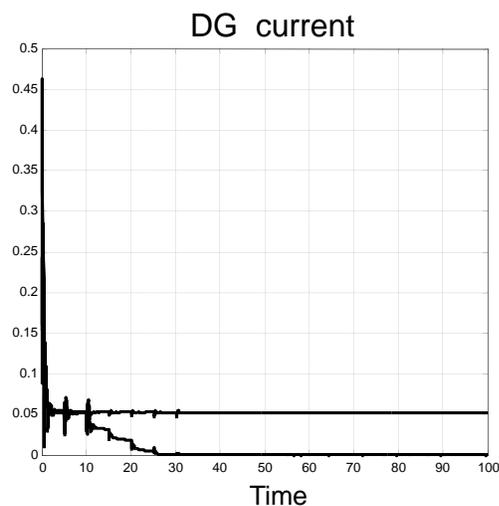

- DG2 position is moved just to the next position of the regulator and DG1 position remains same.
- With higher V_{ref} tap changer takes over from DG in Steady State, but Still available for transient

Region of influence

- The line characteristics and loading determine the strength of influence of voltage controllers
- Integral controllers placed in the zone of strong influence of others can have adverse interaction
- Setting different voltage references of different DGs can play a role for graduated response.


Inherent support from rotary generation

- The internal voltage of generator does not change rapidly, so sudden changes of terminal voltage tend to be limited by internal voltage.
- There will be a transient current overload until the field control acts.
- With inverter there is much lower transient overload capability but faster active control.

Steady State Voltage Support

- The best power factor for DG injection to achieve voltage correction becomes higher for high resistance lines.
- Multiple DG can aid voltage profile of feeder and should provide higher reliability. Setting the voltage references of separate DG's can provide a graduated response to voltage correction.
- Fuel cost is high for synchronous DG. So use reactive power only mode where possible. When extended overload expected commence real power generation.

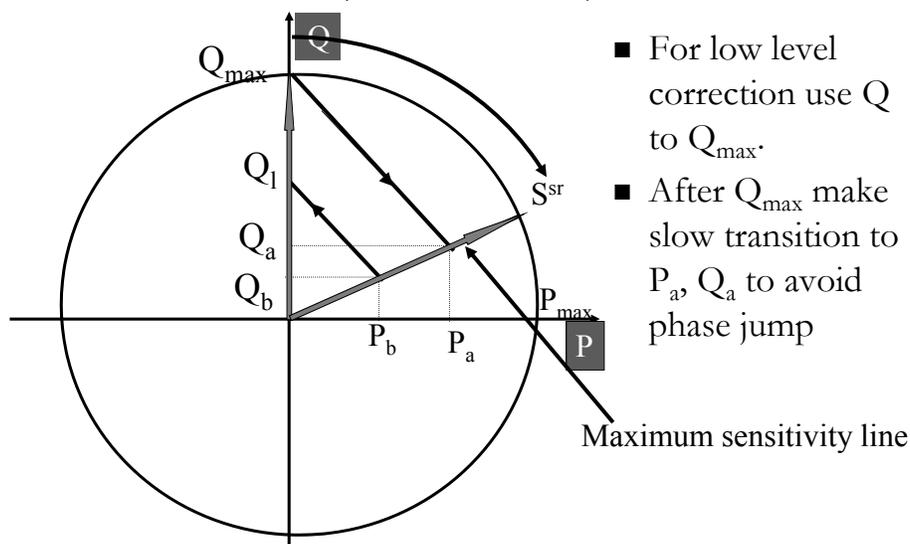Transition from Q Mode to PQ Mode (DG-QPQ)



- For low level correction use Q to Q_{max} .
- After Q_{max} make slow transition to P_a , Q_a to avoid phase jump

Conclusions

- A system with Distributed Generation (DG) has greater load carrying capacity and can support peak-shaving. A network with DG can correct for poor voltage profile, especially needed during peak time of the day.
- DG operation with Q priority is most economical, as it requires generation of less energy and reduces the fuel requirement to meet same level of voltage specification.

Conclusions (Continued)

- ❖ A technique for voltage support using DG system has been presented.
- ❖ A voltage regulation method can be developed based on
 - ❖ Optimal power injection from DG, and
 - ❖ Power output of DG is controlled by the PI controller.
- ❖ Voltage control technique can provide an effective solution for poor voltage problem.